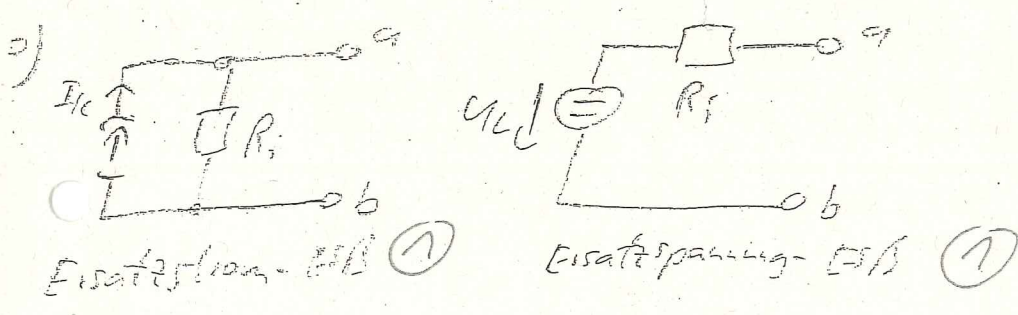



1. a) $Z_i = \frac{1}{5\omega L} + (5\omega L \parallel 5\omega L) + (2R \parallel 2R)$

$= \frac{1}{5\omega L} + 5\omega L + R = R + 5\left(\omega L - \frac{1}{\omega L}\right)$ (2)

b) $\text{Im}\{Z_i\} = 0 \Rightarrow \omega L = \frac{1}{\omega L} \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$ (3)

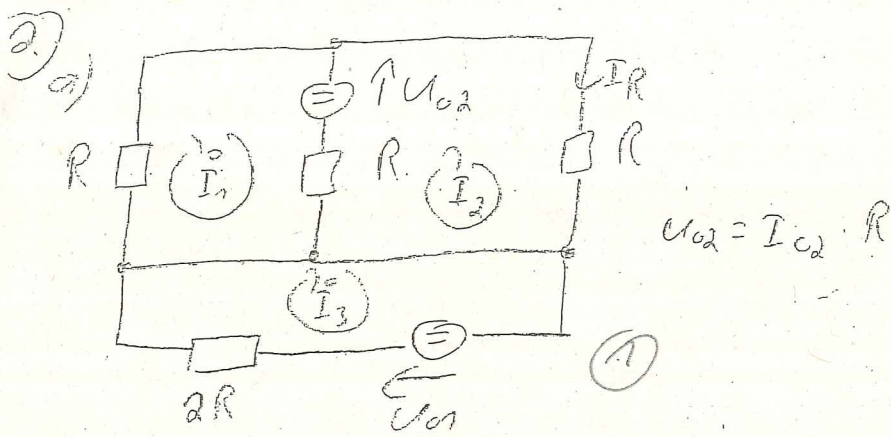c) $R_i = 2R$ (1) d) $u_L = -u_{01}$ (1) $I_{1c} = -\frac{u_{01}}{2R}$ (1)





b)

c) $m = 2 - (4 - 1)$
 $= 2 - (4 - 1) = 1$ (1)

d)

$$\begin{pmatrix} 2R & -R & 0 \\ -R & 2R & 0 \\ 0 & 0 & 2R \end{pmatrix} \begin{pmatrix} \dot{I}_1 \\ \dot{I}_2 \\ \dot{I}_3 \end{pmatrix} = \begin{pmatrix} U_{02} \\ -U_{02} \\ -U_{01} \end{pmatrix} \quad (2)$$

e) $\dot{I}_R = \dot{I}_2$ (1)

f) (i) $4R \cdot \dot{I}_1 - 2R \cdot \dot{I}_2 = 2U_0$ (2)

(ii) $-2R \cdot \dot{I}_1 + 4R \cdot \dot{I}_2 = -2U_0$

(iii) $4R \dot{I}_1 = 2U_0 + 2R \dot{I}_2 \Rightarrow \dot{I}_1 = \frac{2U_0}{4R} + \frac{2R \dot{I}_2}{4R} = \frac{U_0}{2R} + \frac{\dot{I}_2}{2}$

(iv) $-2R \cdot \left(\frac{U_0}{2R} + \frac{\dot{I}_2}{2} \right) + 4R \cdot \dot{I}_2 = -2U_0$

$-U_0 - R \dot{I}_2 + 4R \dot{I}_2 = -2U_0$

$3R \dot{I}_2 = -U_0 =$

$\Rightarrow \underline{\underline{\dot{I}_2}} = -\frac{U_0}{3R} = -\frac{I_0 \cdot R}{3R} = -\frac{300 \text{ mA}}{3} = \underline{\underline{-100 \text{ mA}}}$

3) a)
$$\underline{H'(j\omega)} = \frac{U_2'(j\omega)}{U_1(j\omega)} = \frac{R // (\frac{1}{j\omega C} + j\omega L)}{R + (R // (\frac{1}{j\omega C} + j\omega L))}$$

$$= \frac{\frac{R}{j\omega C} + j\omega RL}{R + \frac{1}{j\omega C} + j\omega L} = \frac{\frac{R}{j\omega C} + j\omega RL}{R^2 + \frac{2R}{j\omega C} + j\omega 2RL}$$

$$= \frac{R - \omega^2 RCL}{2R - \omega^2 RCL + j\omega R^2 C} = \frac{1}{1 + j \frac{\omega R^2 C}{2R - \omega^2 RCL}} \quad (2)$$


b)
$$\underline{Z_{dL}} = \frac{1}{j\omega C} + j\omega L = j \left(\frac{1}{\omega C} \cdot L - \frac{1}{\omega C} \cdot C \right) = j \left(\frac{1}{\omega C} \cdot \omega L - \frac{\omega L}{\omega C} \right) = 0$$

c)
$$\underline{I_R} = 0 \quad (1)$$

d)
$$\underline{I} = \frac{U_1(j\omega)}{R + \underbrace{\frac{1}{j\omega C} + j\omega L}_{=0}} = \frac{U_1}{R} \quad (2)$$

e)
$$\underline{H(j\omega)} = \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{j\omega L}{R + \underbrace{\frac{1}{j\omega C} + j\omega L}_{=0}} = \underline{j \frac{\omega L}{R}} \quad (2)$$


(8)

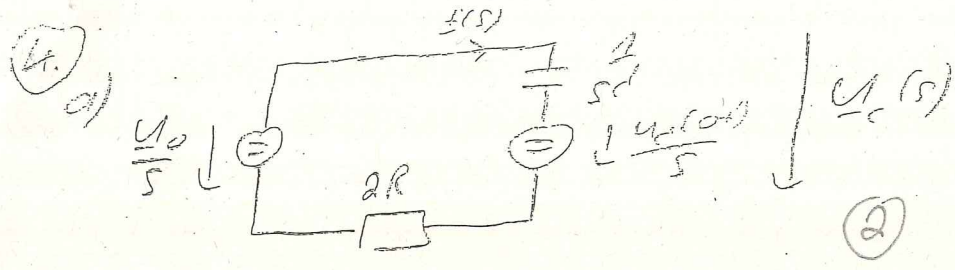

b) Superposition

$$U_c(s) = U_{c1}(s) + U_{c2}(s) \quad (3)$$


• $U_{c1}(s)$ bei $u_c(0^+) = 0$

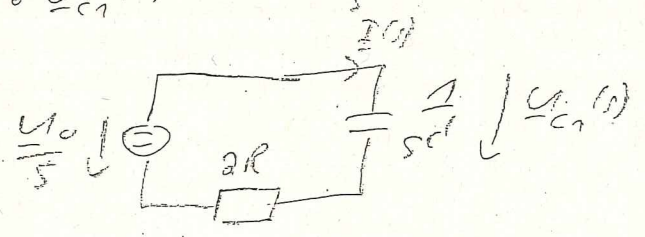

$$\frac{U_{c1}(s)}{\frac{U_0}{s}} = \frac{\frac{1}{sd}}{2R + \frac{1}{sd}}$$

$$\Rightarrow U_{c1}(s) = \frac{U_0}{s} \cdot \frac{1}{2sRd + 1} = U_0 \cdot \frac{\frac{1}{2Rd}}{s(s + \frac{1}{2Rd})}$$


• $U_{c2}(s)$ bei $\frac{U_0}{s} = 0$

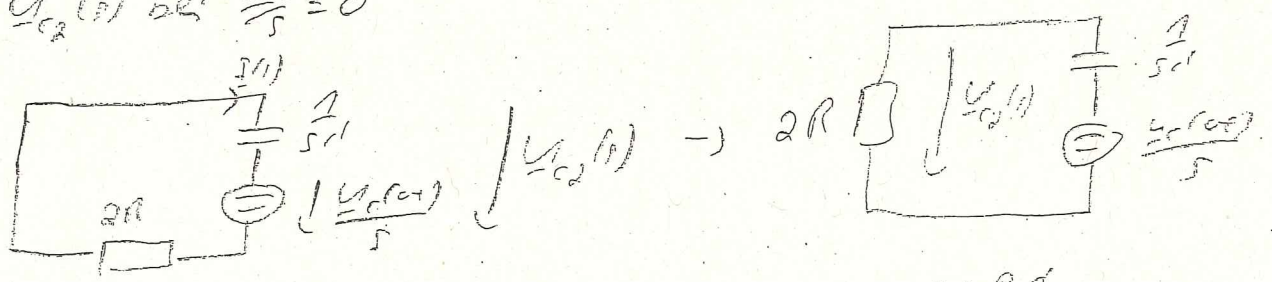

$$\frac{U_{c2}(s)}{\frac{U_c(0^+)}{s}} = \frac{2R}{2R + \frac{1}{sd}} \Rightarrow U_{c2}(s) = \frac{U_c(0^+)}{s} \cdot \frac{2sRd}{2sRd + 1} = U_c(0^+) \cdot \frac{1}{s + \frac{1}{2Rd}}$$

$$U_c(s) = U_{c1}(s) + U_{c2}(s) = U_0 \cdot \frac{\frac{1}{2Rd}}{s(s + \frac{1}{2Rd})} + U_c(0^+) \cdot \frac{1}{s + \frac{1}{2Rd}}$$
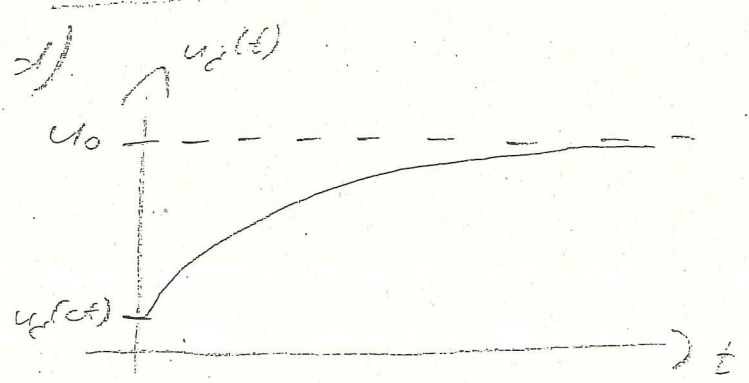
$$U_c(t) = U_0 \cdot (1 - e^{-\frac{1}{2Rd}t}) + U_c(0^+) \cdot e^{-\frac{1}{2Rd}t}; t \geq 0 \quad (2)$$



(7)