

Musterlösung SS 20


1a) $R_i = (R_1 + R_2) \parallel (R_1 + R_2) = \frac{1}{2} (R_1 + R_2)$

b) Netzwerk ist symmetrisch.

$$I_k = 2 \cdot I_0 \frac{R_1}{R_1 + R_2}$$

c) $U_k = I_k \cdot R_i = \cancel{2} I_0 \frac{R_1}{\cancel{R_1 + R_2}} \cdot \frac{1}{\cancel{2}} (\cancel{R_1 + R_2}) = I_0 R_1$

d)

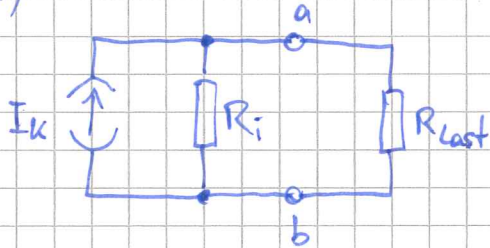

e) Leistungsanpassung: $R_{Last} = R_i = \frac{1}{2} (R_1 + R_2)$

$$I_{Last} = \frac{1}{2} I_k = I_0 \frac{R_1}{R_1 + R_2}$$



$$\Rightarrow U_{Last} = I_{Last} \cdot R_{Last} = I_0 \frac{R_1}{R_1 + R_2} \cdot \frac{1}{2} (R_1 + R_2) = \frac{1}{2} I_0 R_1$$

$$\Rightarrow R_1 = \frac{2 U_{Last}}{I_0} = \frac{2 \cdot 10V}{20mA} = 1 k\Omega$$


$$\Rightarrow R_2 = 2 R_1 = 2 k\Omega$$

2a) $I_2 = \frac{U_{02}}{R}$ $I_3 = \frac{U_{03}}{R}$

b)

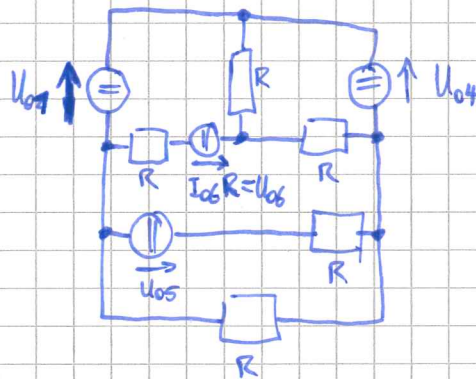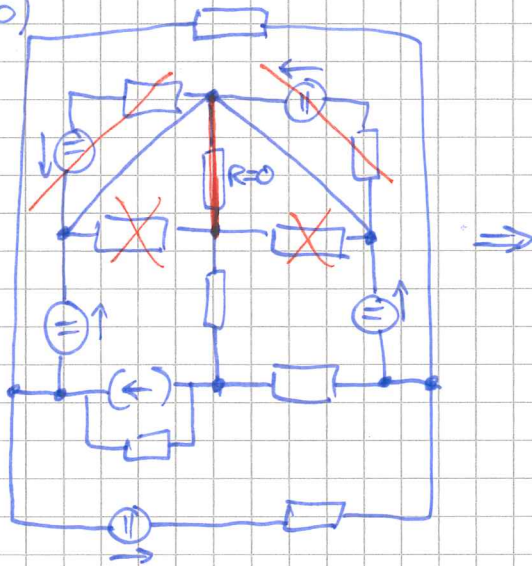

c)

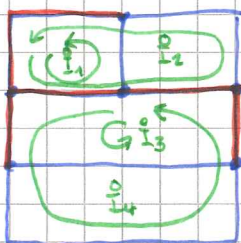

- Graph

- Baum

d)

$$m = z - k + 1$$

$$= 9 - 6 + 1$$

$$= 4$$

$$e) \begin{pmatrix} 2R & R & -R & -R \\ R & 2R & -2R & -2R \\ -R & -2R & 3R & 2R \\ -R & -2R & 2R & 3R \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{pmatrix} = \begin{pmatrix} U_{01} - U_{06} \\ U_{01} - U_{06} - U_{04} \\ U_{06} - U_{05} \\ U_{06} \end{pmatrix}$$

$$f) I_1 = I_1$$

$$g) \begin{pmatrix} 6R & -R \\ -R & 10R \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} U_{03} \\ (I_{01} + I_{02})R - U_{03} \end{pmatrix}$$

$$6R I_1 - R I_2 = U_{03} \Rightarrow I_1 = \frac{U_{03} + R I_2}{6R}$$

$$-R \frac{U_{03} + R I_2}{6R} + 10R I_2 = (I_{01} + I_{02})R - U_{03}$$

$$I_2 \left(10R - \frac{1}{6}R \right) - \frac{1}{6}U_{03} = (I_{01} + I_{02})R - U_{03}$$

$$I_2 = \frac{(I_{01} + I_{02})R - \frac{5}{6}U_{03}}{10R - \frac{1}{6}R}$$

$$= \frac{6(I_{01} + I_{02})R - 5U_{03}}{59R}$$

$$= \frac{6}{59} (I_{01} + I_{02}) - \frac{5U_{03}}{59R}$$

$$= \frac{6}{59} (50\text{mA} + 50\text{mA}) - \frac{5 \cdot 10\text{V}}{59 \cdot 1\text{k}\Omega}$$

$$= 9,32\text{ mA}$$

$$I_1 = \frac{10\text{V} + 1\text{k}\Omega \cdot 9,32\text{mA}}{6 \cdot 1\text{k}\Omega} = 3,22\text{ mA}$$

$$3a) H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{\frac{1}{j\omega C}}{2R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega 2RC}$$

$$b) |H(j\omega)| = \frac{1}{\sqrt{1 + 4\omega^2 R^2 C^2}}$$

$$c) |H(j\omega=0)| = 1$$

$$|H(j\omega \rightarrow \infty)| = 0$$

$$b) \varphi(\omega) = -\arctan(2\omega RC)$$

$$c) \varphi(\omega=0) = 0$$

$$\varphi(\omega \rightarrow \infty) = -90^\circ$$


\Rightarrow Übertragungsverhalten: Tiefpass

$$d) |H(j\omega)| = \frac{H_{\max}}{\sqrt{2}} = \frac{1}{\sqrt{1 + 4\omega^2 R^2 C^2}} \quad |H_{\max} = 1$$

$$\Rightarrow 4\omega_g^2 R^2 C^2 = 1$$

$$\Rightarrow \omega_g = \frac{1}{2RC}$$

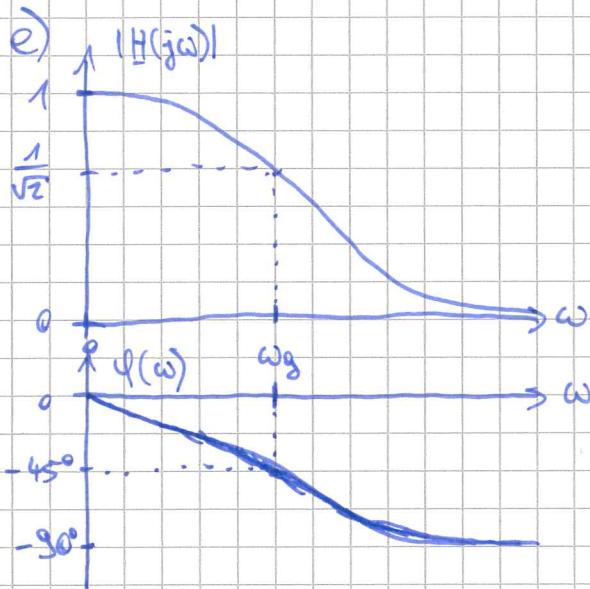
$$\varphi(\omega_g) = -\arctan\left(\cancel{2} \cdot \frac{1}{\cancel{2RC}} \cdot RC\right) = -\arctan(1) = -45^\circ$$



$$f) |H'(j\omega=0)| = 0$$

$$|H'(j\omega \rightarrow \infty)| = 1$$
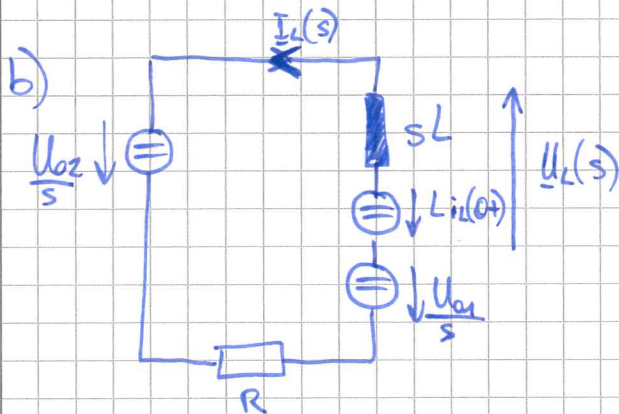
$$4a) i_L(t=0^-) = i_L(t=0^+) = \frac{U_{01}}{R}$$



$$c) \underline{I}_L(s) = \frac{-\frac{U_{02}}{s} + L i_L(0^+) + \frac{U_{01}}{s}}{R + sL} = \frac{sL i_L(0^+) + U_{01} - U_{02}}{s(R + sL)}$$

$$= \frac{L i_L(0^+)}{R + sL} + \frac{U_{01} - U_{02}}{s(R + sL)} = \frac{U_{01}}{R} \frac{1}{s + \frac{R}{L}} + \frac{U_{01} - U_{02}}{R} \cdot \frac{R/L}{s(s + R/L)}$$

$$\begin{aligned}
 d) \quad i_L(t) &= \frac{U_{01}}{R} \cdot e^{-\frac{R}{L}t} + \frac{U_{01} - U_{02}}{R} (1 - e^{-\frac{R}{L}t}) ; t \geq 0 \\
 &= \frac{U_{01}}{R} \cdot \cancel{e^{-\frac{R}{L}t}} + \frac{U_{01}}{R} - \frac{U_{02}}{R} - \frac{U_{01}}{R} \cancel{e^{-\frac{R}{L}t}} + \frac{U_{02}}{R} e^{-\frac{R}{L}t} ; t \geq 0 \\
 &= \frac{U_{01}}{R} - \frac{U_{02}}{R} (1 - e^{-\frac{R}{L}t}) ; t \geq 0
 \end{aligned}$$

$$e) \quad i_L(t_0) = \frac{U_{01}}{R} - \frac{U_{02}}{R} (1 - e^{-\frac{R}{L}t_0}) \stackrel{!}{=} 0$$

$$U_{01} = U_{02} (1 - e^{-\frac{R}{L}t_0})$$

$$\frac{U_{01}}{U_{02}} = 1 - e^{-\frac{R}{L}t_0}$$

$$e^{-\frac{R}{L}t_0} = \frac{U_{02} - U_{01}}{U_{02}}$$

$$-\frac{R}{L}t_0 = \ln\left(\frac{U_{02} - U_{01}}{U_{02}}\right)$$

$$t_0 = -\frac{L}{R} \ln\left(\frac{U_{02} - U_{01}}{U_{02}}\right)$$

$$= -\frac{9,276 \text{ H}}{500 \Omega} \ln\left(\frac{12 \text{ V} - 5 \text{ V}}{12 \text{ V}}\right)$$

$$= 10 \text{ ms}$$

$$f) \quad i_L(0) = \frac{U_{01}}{R} = 10 \text{ mA}$$

$$i_L(t \rightarrow \infty) = -14 \text{ mA}$$

$$i_L(10 \text{ ms}) = 0$$

