


1.)

a)

$$R_i = ((R \parallel R) + R) \parallel R$$

$$= \frac{(\frac{R}{2} + R) \cdot R}{\frac{R}{2} + R + R} = \underline{\underline{\frac{3}{5} R}}$$


b) $I_k = I_{k1} + I_{k2}$

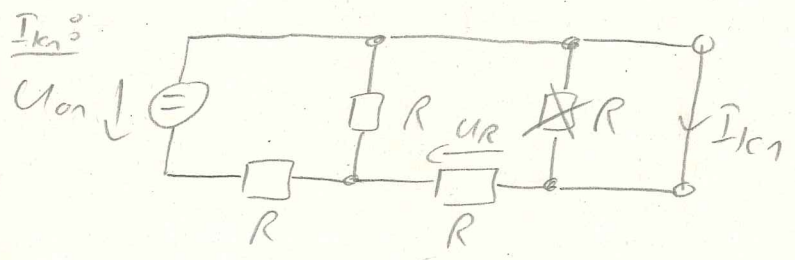

$U_R = \frac{R \cdot R}{R + R} = \frac{R}{2}$

$$\frac{U_R}{U_{01}} = \frac{\frac{R \cdot R}{R + R}}{R + \frac{R \cdot R}{R + R}} = \frac{\frac{R}{2}}{R + \frac{R}{2}} \Rightarrow U_R = \frac{1}{3} U_{01}$$

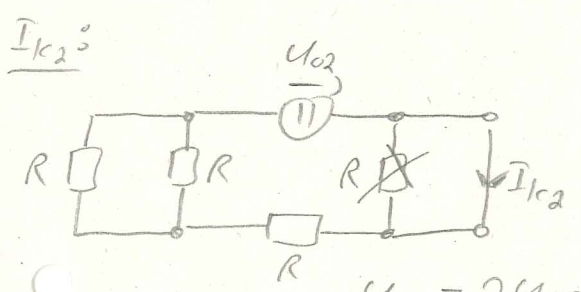
$I_{k1} = \frac{U_R}{R} = \underline{\underline{\frac{U_{01}}{3R}}}$



$I_{k2} = - \frac{U_{02}}{\frac{R}{2} + R} = - \frac{U_{02}}{\frac{3}{2} R}$

$I_k = I_{k1} + I_{k2} = \underline{\underline{\frac{U_{01} - 2U_{02}}{3R}}}$

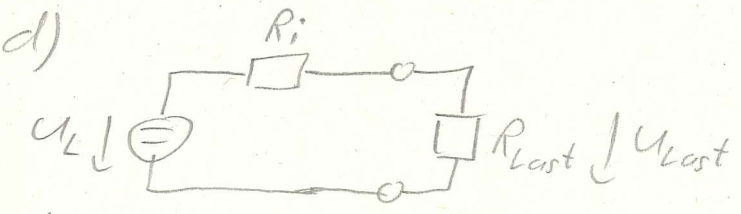c) $U_L = I_k \cdot R_i = \frac{U_{01} - 2U_{02}}{3R} \cdot \frac{3}{5} R = \underline{\underline{\frac{U_{01} - 2U_{02}}{5}}}$




e) Leistungsanpassung: $R_{Last} = R_i$

$\frac{U_{Last}}{U_L} = \frac{R_{Last}}{R_i + R_{Last}} = \frac{1}{2} \Rightarrow U_{Last} = \frac{1}{2} \cdot \frac{U_{01} - 2U_{02}}{5} = \underline{\underline{\frac{U_{01} - 2U_{02}}{10}}}$


$$\underline{\underline{P_{last} = \frac{U_{last}^2}{R_{last}} = \frac{\left(\frac{U_{01} - 2U_{02}}{10}\right)^2}{\frac{3}{5}R}}}$$

2. a)

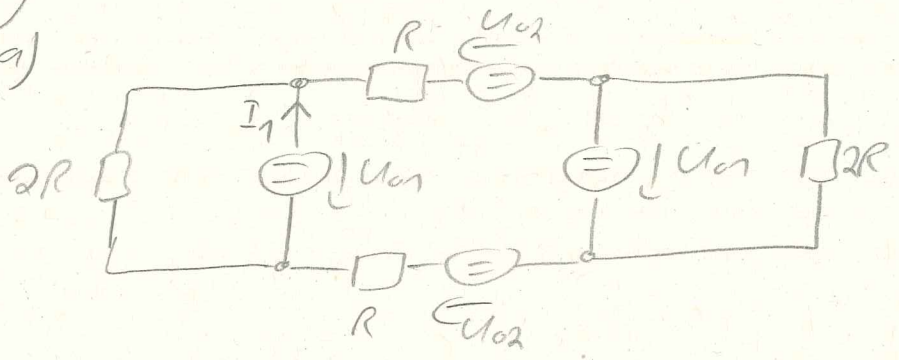

$$\underline{\underline{U_{02} = R \cdot I_{02}}}$$

b)

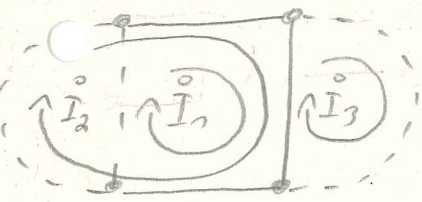

$$c) \quad m = 2 - (k - 1) = \underline{\underline{3}}$$

d)

$$\begin{pmatrix} 2R & 2R & 0 \\ 2R & 4R & 0 \\ 0 & 0 & 2R \end{pmatrix} \begin{pmatrix} \overset{\circ}{I}_1 \\ \overset{\circ}{I}_2 \\ \overset{\circ}{I}_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -U_{01} \\ U_{01} \end{pmatrix}$$

e) $I_1 = \overset{\circ}{I}_1$

I: $2R \overset{\circ}{I}_1 + 2R \overset{\circ}{I}_2 = 0$

II: $2R \overset{\circ}{I}_1 + 4R \overset{\circ}{I}_2 = -U_{01}$

III: $2R \overset{\circ}{I}_3 = U_{01}$

IV: $\overset{\circ}{I}_2 = -\overset{\circ}{I}_1$


in II: $2R \overset{\circ}{I}_1 - 4R \overset{\circ}{I}_1 = -U_{01}$

(I) $-2R \overset{\circ}{I}_1 = -U_{01}$

(II) $\overset{\circ}{I}_1 = \frac{U_{01}}{2R}$

$\Rightarrow I_1 = \overset{\circ}{I}_1 = \frac{U_{01}}{2R} = \frac{1V}{2k\Omega} = \underline{\underline{0,5mA}}$

3.

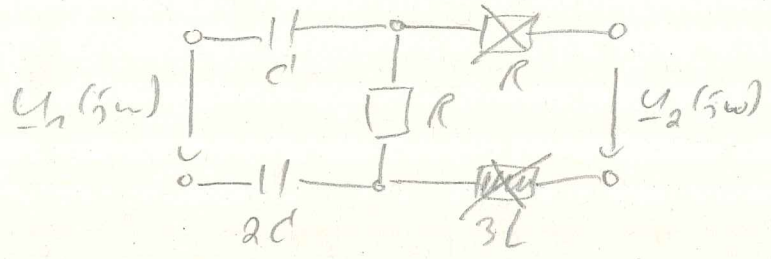

a)
$$\underline{H(s)} = \frac{U_2(s)}{U_1(s)} = \frac{R}{\frac{1}{sC} + \frac{1}{s3L} + R} = \frac{R}{\frac{3}{s2dR} + R} = \frac{1}{1 - j \frac{3}{\omega 2dR}}$$

b)
$$|H(s)| = \frac{1}{\sqrt{1 + \left(\frac{3}{\omega 2dR}\right)^2}}, \quad \varphi(\omega) = \arctan\left(\frac{3}{\omega 2dR}\right)$$



c)
$$\omega \rightarrow 0: |H(s)| = 0, \quad \varphi(\omega) = \frac{\pi}{2}$$

$$\omega \rightarrow \infty: |H(s)| = 1, \quad \varphi(\omega) = 0$$

$$\omega = \omega_g: |H_{max}| = |H(s_{\omega_g})| \Rightarrow \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{3}{\omega_g 2dR}\right)^2}}$$


$$\Rightarrow \omega_g = \frac{3}{2dR}$$
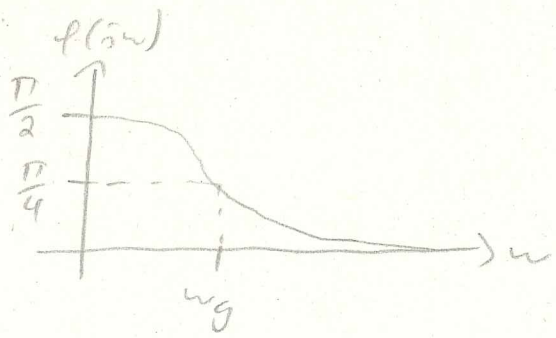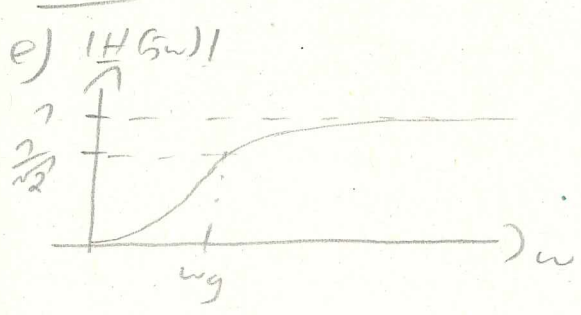
$$\varphi(\omega_g) = \arctan(1) = \frac{\pi}{4}$$



f) Hochpass!

4. a) $u_c(t=0^-) = u_c(t=0^+) = U_0$

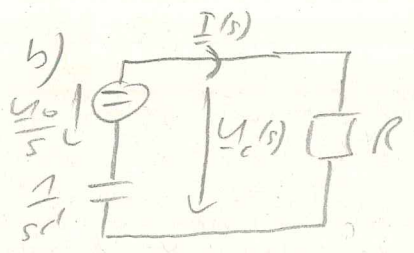


c) $\frac{u_c(s)}{\frac{U_0}{s}} = \frac{R}{\frac{1}{sd} + R} \Rightarrow u_c(s) = U_0 \cdot \frac{1}{s + \frac{1}{Rd}}$

d) $u_c(t) = U_0 \cdot e^{-\frac{1}{Rd}t}; t \geq 0$

e) $u_c(t=T^-) = u_c(t=T^+) = 0$

f) $T \rightarrow \infty$:

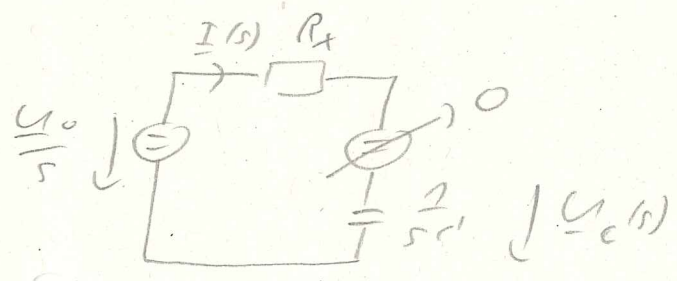

g) $\frac{u_c(s)}{\frac{U_0}{s}} = \frac{1}{sd} \cdot \frac{1}{\frac{1}{sd} + R_x} \Rightarrow u_c(s) = U_0 \cdot \frac{1}{s(s + \frac{1}{dR_x})} \cdot e^{-sT}$

h) $u_c(t) = U_0 \cdot (1 - e^{-\frac{1}{dR_x}(t-T)}) = U_0 - U_0 \cdot e^{-\frac{1}{dR_x}(t-T)}; t \geq T$

